

# LRC AC Circuits

## 1 Introduction

Previously, we have examined circuits with either capacitors and resistors or inductors and resistors powered by batteries that produce constant voltage. These are called direct current (DC) circuits. When a switch was closed to complete a circuit, the current varied in time, and the time dependence was exponential (the current had a term  $e^{-t/\tau}$ ).


If we use a voltage source that varies in time sinusoidally instead of a battery, the current will also vary in time sinusoidally, possibly with a different phase. There will also be a “transient” exponential variation for a short amount, but here we only discuss the variation after the transient variation is zero “steady state.”

### 1.1 R Only


Figure (a) below shows a circuit in which an AC power source causes the current to vary sinusoidally in time according to  $i(t) = I \cos(\omega t)$ . By Ohm’s law, the equation for the instantaneous voltage across the resistor is  $v_R(t) = IR \cos(\omega t) = V_R \cos(\omega t)$ , where  $V_R$  is the amplitude of the voltage source.

Figure (b) shows the time variation of current and voltage for this circuit. The voltage and current are “in phase” because the peaks, valleys, and zero crossings of  $i(t)$  and  $v_R(t)$  occur at the same time.

(a) Circuit with ac source and resistor

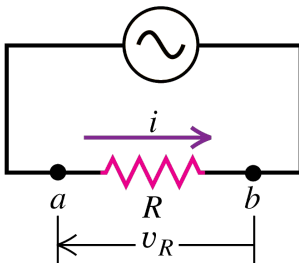

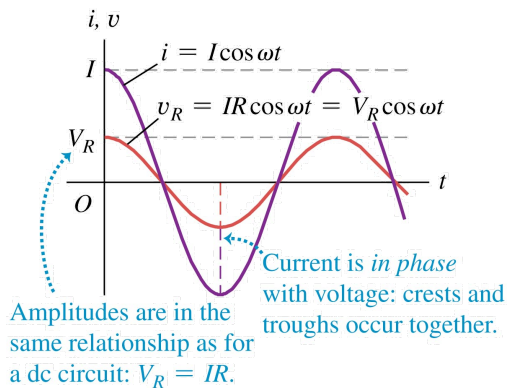(b) Graphs of current and voltage versus time



## 1.2 L Only


Figure (a) below shows a  $RL$  circuit in which an AC power source causes the current to vary sinusoidally in time according to  $i(t) = I \cos(\omega t)$ .

The voltage across the inductor varies in time according to  $v_L(t) = I\omega L \cos(\omega t + 90^\circ)$ .

The term  $\omega L$  is called the inductive reactance:  $X_L \equiv \omega L$ , which has units of Ohms when  $L$  has units of H and  $\omega$  has units of rad/s. With this new variable,  $v_L(t) = IX_L \cos(\omega t + 90^\circ)$ .


Figure (b) shows the  $v(t)$  and  $i(t)$ . The voltage across the inductor “leads” the current by  $90^\circ$  (or, equivalently,  $T/4$ , where  $T = 2\pi/\omega$ ) because the maxima (or minima) in  $v_L(t)$  occur before the maxima (or minima) in  $i(t)$ .
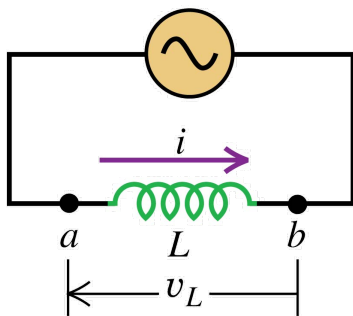
### (a) Circuit with ac source and inductor



© 2016 Pearson Education, Inc.
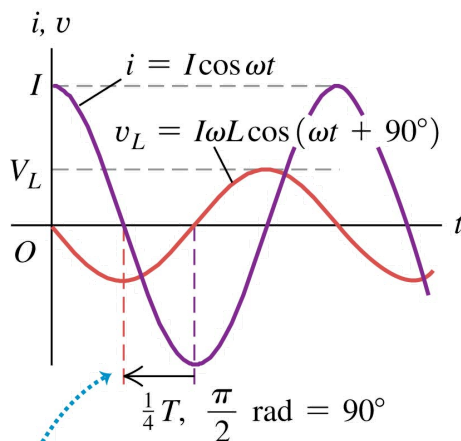
### (b) Graphs of current and voltage versus time



Voltage curve *leads* current curve by a quarter-cycle (corresponding to  $\phi = \pi/2$  rad =  $90^\circ$ ).

© 2016 Pearson Education, Inc.

### 1.3 C Only


Figure (a) below shows a  $RC$  circuit in which an AC power source causes the current to vary sinusoidally in time according to  $i(t) = I \cos(\omega t)$ .

The voltage across the capacitor varies according to  $v_C(t) = \frac{I}{\omega C} \cos(\omega t - 90^\circ)$ .

The term  $1/(\omega C)$  is called the capacitive reactance:  $X_C \equiv 1/(\omega C)$ . With this new variable,  $v_C(t) = IX_C \cos(\omega t - 90^\circ)$ .


Figure (b) shows the  $v(t)$  and  $i(t)$ . The voltage across the inductor “lags” the current by  $90^\circ$  (or, equivalently,  $T/4$ ) because the maxima (or minima) in  $v_C(t)$  occur after the maxima (or minima) in  $i(t)$ .

(a) Circuit with ac source and capacitor

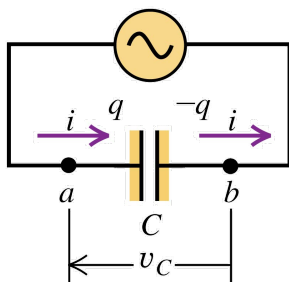

© 2016 Pearson Education, Inc.

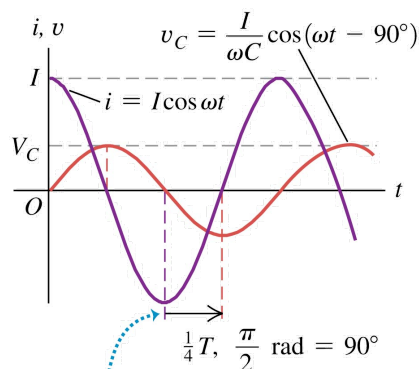(b) Graphs of current and voltage versus time



Voltage curve *lags* current curve by a quarter-cycle (corresponding to  $\phi = -\pi/2$  rad =  $-90^\circ$ ).


© 2016 Pearson Education, Inc.

## 1.4 Series LRC circuit

---

Suppose that we know the current  $i(t)$  in the following series LRC circuit is  $i(t) = I \cos(\omega t)$ .

(a)  $L$ - $R$ - $C$  series circuit

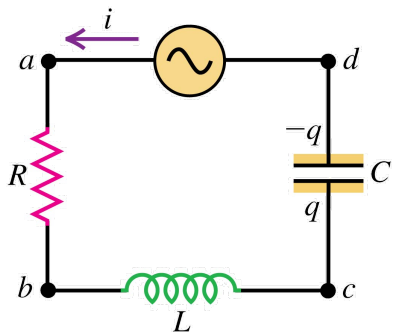

We want to know the voltage across the AC power supply,  $v_d - v_a$ , which we call  $v$ . We know the voltage across each of the components from the discussion above:

$$v_R(t) = IR \cos(\omega t)$$

$$v_L(t) = I\omega L \cos(\omega t + 90^\circ) = IX_L \cos(\omega t + 90^\circ)$$

$$v_C(t) = \frac{I}{\omega C} \cos(\omega t - 90^\circ) = IX_C \cos(\omega t - 90^\circ)$$

From Kirchhoff's voltage law:

$$v(t) - v_R(t) - v_L(t) - v_C(t)$$

Substitution gives

$$v(t) = IR \cos(\omega t) + IX_L \cos(\omega t + 90^\circ) + IX_C \cos(\omega t - 90^\circ)$$


In this activity, you will compute  $v(t)$  in two ways. First, you will use the above formula and a trig identity to write  $v(t)$  in the form  $IZ \cos(\omega t + \phi)$ , where the constants  $Z$  and  $\phi$  depend on  $R$ ,  $L$ , and  $C$  (or equivalently,  $R$ ,  $X_L$ , and  $X_C$ ). Next, you will use a general formula to compute  $Z$  and  $\phi$ .

## 2 Problem I

---

A series LRC circuit with known values of  $I$ ,  $R$ ,  $L$ , and  $C$  are such that  $IR = 1$  [V],  $IX_L = 1$  [V], and  $X_C = 0$ . In addition, assume  $i(t) = (1 \text{ A}) \cos \omega t$  and  $\omega = 2\pi \text{ s}^{-1}$ .

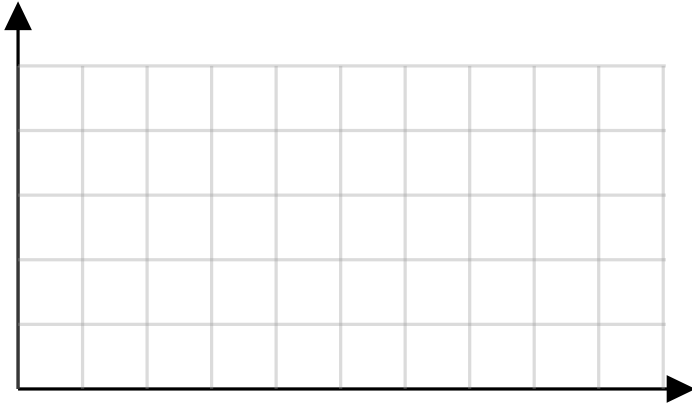Plot all quantities requested below on the same graph.



1. Plot  $i(t)$
2. Compute the period,  $T$ , of  $i(t)$
3. Plot  $v_R(t)$ ,  $v_L(t)$ , and  $v_C(t)$
4. Starting with  $v(t) = v_R(t) + v_L(t) + v_C(t)$ , use the trig identity
$$A \cos(\theta) + B \cos(\theta + \pi/2) = \sqrt{A^2 + B^2} \cos(\theta + \tan^{-1}(B/A))$$
to write  $v(t)$  in the form  $v(t) = Z \cos(\omega t + \phi)$ .  
That is, find the constants  $Z$  and  $\phi$ .
5. Plot  $v(t)$

### 3 Problem II

---

In the previous problem, computing  $v(t)$  required the use of a trig identity to combine  $v_R$  and  $v_L$  and write  $v(t)$  in the form  $v(t) = Z \cos(\omega t + \phi)$ , where  $Z$  and  $\phi$  are constants that depend on  $L$  and  $R$ . When  $v_C$  is not zero, additional algebra is needed to compute  $v(t)$  (by using the trig identity again). However, there is a formula that can be used to find  $v(t)$  in general so that trig identities are not needed.

It can be shown that in general, the voltage across the AC power source in a RLC circuit when  $i(t) = I \cos \omega t$  is

$$v(t) = IZ \cos(\omega t + \phi)$$

Where the series LRC impedance  $Z$  is defined as

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

and

$$\phi = \tan^{-1} \left( \frac{X_L - X_C}{R} \right) = \tan^{-1} \left( \frac{\omega L - \frac{1}{\omega C}}{R} \right)$$

When  $\phi$  is positive,  $v(t)$  leads  $i(t)$ . When  $\phi$  is negative,  $v(t)$  lags  $i(t)$ . When  $\phi = 0$ ,  $v(t)$  is in phase with  $i(t)$ .

1. Using the parameters given in the previous problem, find  $v(t)$  using the above formula.
2. Suppose  $X_C$  is not zero. What is the relationship between  $\omega$ ,  $L$ , and  $C$  such that the voltage and current in the circuit is in phase?